
# Project 1 Milk Overflow Alarm

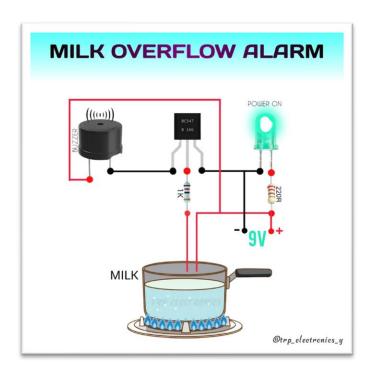

# Components Required

- 1 × BC547 Transistor
- 1 × Buzzer (5V/9V)
- 1 × Indicator LED (Red or Green)
- $1 \times \text{Resistor}$  (220 $\Omega$  for LED,  $10\text{k}\Omega$  for base bias)
- 1 × 9V Battery + Battery Clip
- Connecting Wires
- 2 × Crocodile Clips (to attach with milk container)
- Small Base/Board to mount the circuit

### Circuit Diagram



## Working Principle

The Milk Overflow Alarm works on the conductivity of milk.

- Two wires with crocodile clips are placed in the milk container.
- One wire is attached slightly lower, and the other wire is placed at the top level where you want to detect overflow.
- When the milk rises and touches both wires, a small current flows through the milk (since milk is a conductor).
- This current goes to the base of the BC547 transistor, turning it ON.
- As a result, the buzzer and LED get activated, giving an alarm that the milk is about to overflow.

### Connections

### Connections (Step by Step)

- 1. **Battery (9V)**  $\rightarrow$  Connect negative terminal to ground (common line).
- 2. Transistor BC547
  - $\circ$  Emitter (E) → Connect to ground.
  - $\circ$  Collector (C)  $\rightarrow$  Connect one end of the buzzer + LED.
  - o **Base (B)**  $\rightarrow$  Connect with one end of the sensing wire (via 1kΩ resistor).

### 3. Buzzer + LED

- $\circ$  Other end of **buzzer and LED**  $\rightarrow$  Connect to +9V supply.
- $\circ$  (Use 220 $\Omega$  resistor in series with LED).

### 4. Sensing Wires with Crocodile Clips

- o One clip → Connect directly to +9V battery.
- Second clip  $\rightarrow$  Connect to transistor base (through 1kΩ resistor).
- Mount clips in milk container:
  - First wire (grounded) at bottom/side.
  - Second wire just above the desired milk level.
- 5. When milk touches both wires → small current flows → transistor turns ON → LED + buzzer activate.

### Applications

- Useful in homes to prevent milk overflow while boiling.
- Can also be used for liquid level detection in tanks.

### Advantages

- · Very simple and low-cost project.
- Easy to build for beginners.
- Runs on a 9V battery (safe to use).

### Possible Upgrades / Modifications

- Along with buzzer and LED, you can connect a **relay + small water pump**.
  - When milk reaches the top level, instead of just giving an alarm, the circuit can automatically activate the pump to drain excess milk and prevent overflow.
- You can replace the buzzer with a **flashing high-brightness LED** for silent indication.
- You can power the circuit using a **USB 5V adapter** instead of a 9V battery for long-term usage.
- Add a **latching circuit** so that even if the milk level drops, the buzzer keeps ringing until manually reset.
- Upgrade using a **microcontroller (Arduino)** to display "Milk Overflow" on an LCD screen.

